

INDEX

1. SEMICONDUCTORS

- EOS 1.2 NTC-resistor
- EOS 1.3 Light dependent resistor (LDR)
- EOS 1.4 Measuring the luminous intensity

2. DIODES

- EOS 2.1 Silicon diode
- EOS 2.2 Forward voltage of a silicon diode
- EOS 2.2.1 Characteristic lines of semiconductor diodes
- EOS 2.3 Diodes protect meters
- EOS 2.4 Light-emitting diode (LED)
- EOS 2.4.1 Forward voltage of an LED
- EOS 2.5 Polarity indicators
- EOS 2.5.1 Polarity indicators at AC with variable frequency
- EOS 2.6 Zener diodes
- EOS 2.7 Stabilizing of voltage

3. TRANSISTORS

- EOS 3.1 Does a transistor consist of two diodes?
- EOS 3.2 Base current makes collector current possible (NPN-transistor)
- EOS 3.3 The transistors as an amplifier
- EOS 3.3.6 Transfer characteristic of a NPN-transistor
- EOS 3.4 Light triggered alarm
- EOS 3.5 Base voltage divider
- EOS 3.6 Construction of a burglar alarm by means of trip wire
- EOS 3.7 Automatic illumination
- EOS 3.8 Alarm by means of light barriers
- EOS 3.9 Fire alarm
- EOS 3.10 Electric thermometer

4. CONDENSERS

- EOS 4.1 A storage for electric charges
- EOS 4.2 A condenser supplies base current
- EOS 4.3 Capacitance
- EOS 4.3.1 Time switch
- EOS 4.4 A condenser blocks D.C
- EOS 4.5 Half-wave rectification
- EOS 4.6 Smoothing of rectified voltage
- EOS 4.7 Condensers as A.C. resistance
- EOS 4.8 Charged capacitors connected in series

5. RECTIFICATION

- EOS 5.3 Bridge connection
- EOS 5.3.1 Bridge connection at A.C. with variable frequency

6. MULTIVIBRATOR

- EOS 6.2 Discharging of a condenser
- EOS 6.3 A condenser prevents base current

INDEX

9. LOGIC CIRCUITS

EOS 9.1	The logic AND-circuit
EOS 9.2	The logic OR-circuit
EOS 9.3	The logic NOT-circuit
EOS 9.4	AND-circuit
EOS 9.5	OR-circuit
EOS 9.6	NOT-circuit
EOS 9.7	NAND-circuit
EOS 9.8	NOR-circuit